

Electricity – Apple-level

How do we use electricity in our everyday life?

Materials:

Batteries (1,5V (AA) or 9V battery)

Leads with adapters

Small light bulbs (6V – 0,5 A/1,0A)

Holders for the light bulbs

Tin foil

What to do:

Connect the batteries with the light bulb to turn on the light



What did you do?

What did you find out?

Is it possible to use the tin foil instead for the leads? Why/why not?